

ENGRD 2300

Introduction to Digital Logic Design

Fall 2009

Verilog



Cornell University

Announcements

- **Prelim 1**
 - Being graded...
- **Regrade Procedure**
 - Fill out the regrade request form within one week
- **HW4 to be posted soon**

Readings

- **Sections 7.1-7.8**
- **Sections 5.1, 5.4, 7.13 (Today)**
 - Now's the time to worry about the HDL (Verilog) stuff
 - I.e., Review Verilog parts of Ch 6
- **Sections 8.1, 8.4 – 8.5 (Thursday)**


Hardware Description Languages

- **Why use an HDL?**
 - Describe complex designs (millions of gates)
 - Input to synthesis tools (synthesizable subset)
 - Design exploration with simulation
- **Why not use a general purpose language?**
 - Support for structure and instantiation
 - Support for describing bit-level behavior
 - Support for timing
 - Support for concurrency
- **Verilog vs. VHDL (VHSIC HDL)**
 - Verilog is relatively simple and close to C
 - VHDL is close to Ada (DoD-sponsored language)
 - Verilog has 50% of the world digital design market (larger share in US)

Not a Programming Language

- With every keystroke say, “I’m designing hardware”
- Concurrent language
 - $a \leq \sim b;$
 - $c \leq d;$
 - Which happens first?
- Warnings
 - It’s easy to create tons of hardware
 - It’s easy to create descriptions that can’t be synthesized

HDL-based design flow

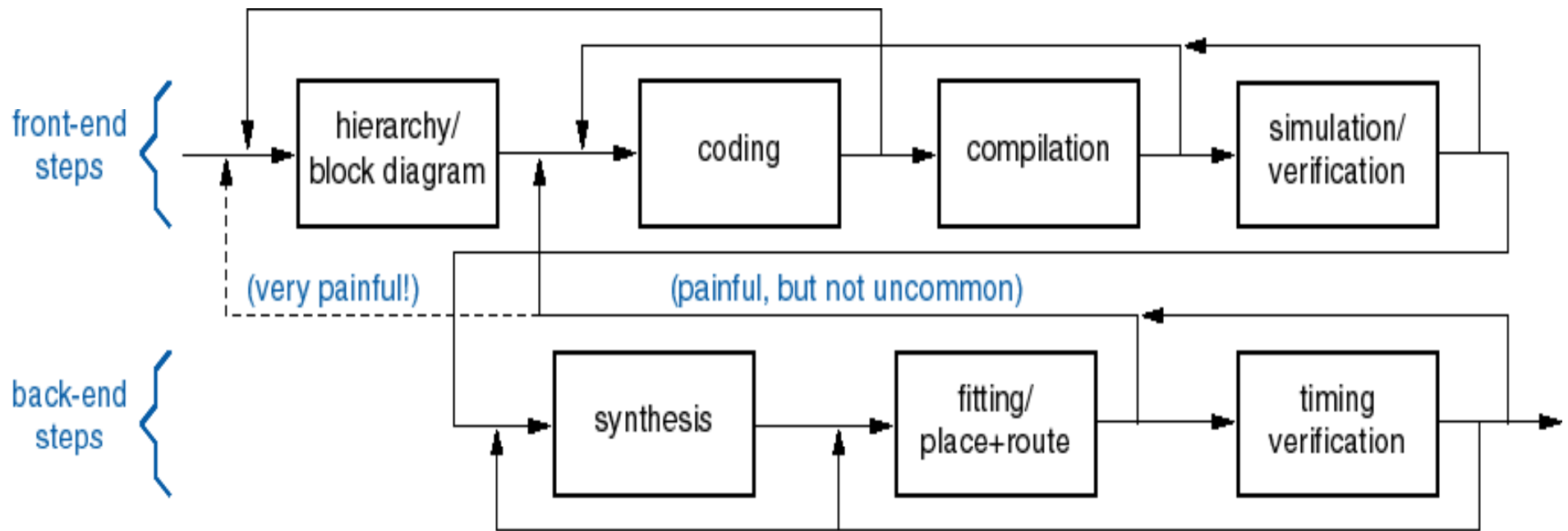


- Back-end differs by target technology
 - May be PLD, CPLD, FPGA, or ASIC
- For ASICs, verification and fitting phases are usually much longer (as a fraction of overall project time)

Verilog


- **Developed in the early 1980s by Gateway Design Automation (later bought by Cadence)**
 - Syntactically similar to C
 - Shares market 50/50 with VHDL
- **Used for design description, simulation, and synthesis**
 - Synthesis became practical in the early 90s and use of VHDL and Verilog has taken off since then
- **Note that only a subset of the language can be synthesized**
 - Easy to code something that can't be synthesized
 - Try to distinguish, which is which!

Verilog Program Structure

 - **System is a collection of modules**
 - Module corresponds to a single piece of hardware
- **Declarations**
 - Describe names and types of inputs and outputs
 - Describe local signals, variables, constants, etc.
- **Statements specify what the module does**



Verilog Hierarchy

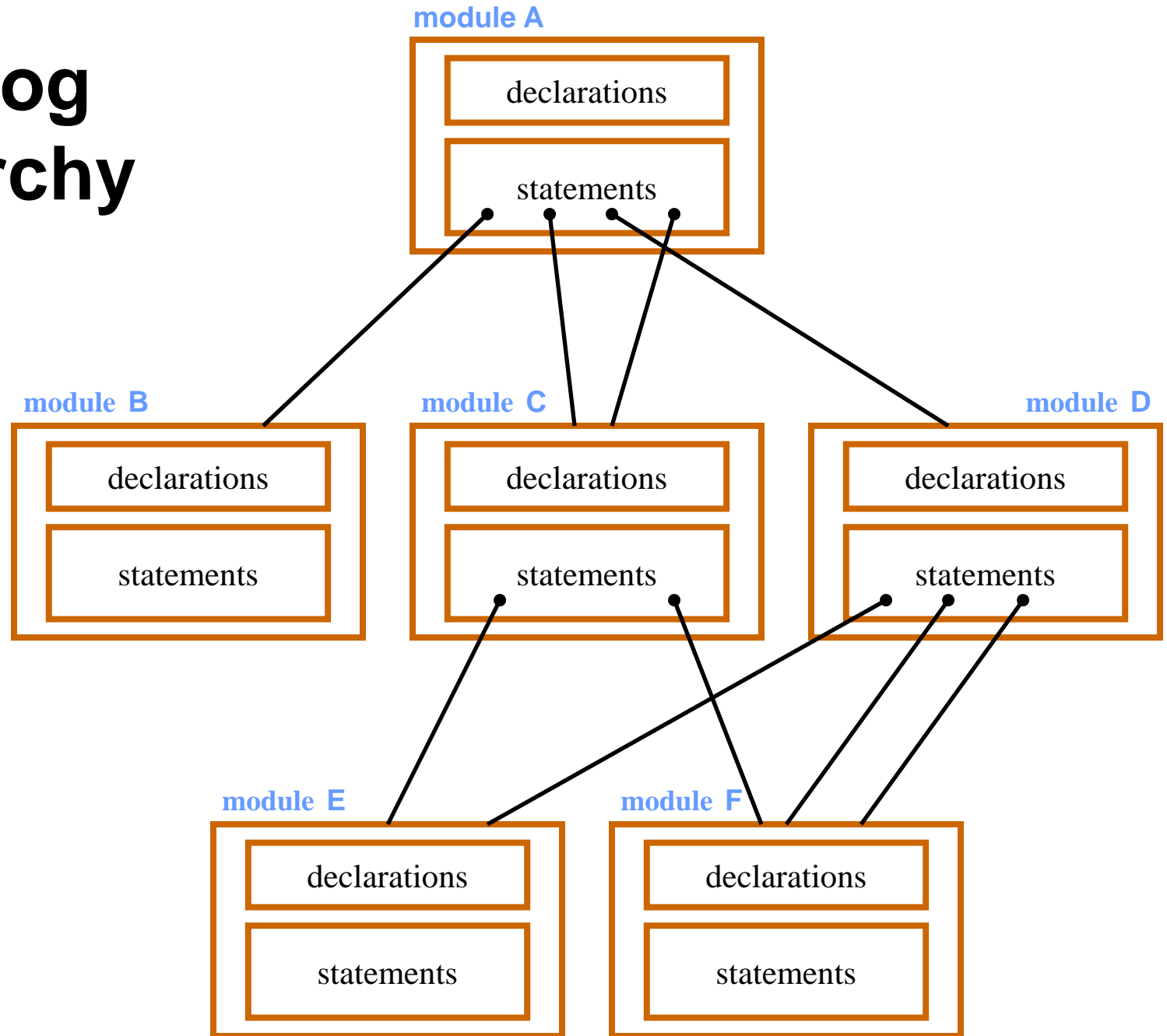

Verilog Program Structure

```
module V2to4dec( i0,i1,en,y0,y1,y2,y3 );
```

```
  input i0,i1,en;
```

```
  output y0,y1,y2,y3;
```

```
  wire noti0,noti1;
```

Declarations

```
  not U1(noti0,i0);
```

```
  not U2(noti1,i1);
```

```
  and U3(y0,noti0,noti1,en);
```


```
  and U4(y1,  i0,noti1,en);
```

```
  and U5(y2,noti0,  i1,en);
```

```
  and U6(y3,  i0,  i1,en);
```

```
endmodule
```

Statements

 

Verilog Signals

- Verilog signals can have 1 of 4 values

0 Logical 0, or false

1 Logical 1, or true

x Unknown logical value

z High impedance

- Bitwise Boolean Operators

& AND

| OR

^ Exclusive OR

^~ Exclusive NOR

~ NOT

A	B	A & B
0	0	0
0	1	0
0	x	0
0	z	0
1	0	0
1	1	1
1	x	x
1	z	x
x	0	0
x	1	x
x	x	x
x	z	x
z	0	0
z	1	x
z	x	x
z	z	x

Logic Operations with Signals

- **Example:**

$0 \mid x = ?$ (x)

$0 \mid z = ?$ (x)

$1 \mid x = ?$ (1)

$1 \mid z = ?$ (1)

$x \mid x = ?$ (x)

$x \mid z = ?$ (x)

$z \mid z = ?$ (x)

Verilog Nets

- **Two types of signals**
 - Nets and Variables
- **A *net* roughly corresponds to a wire in a circuit**
 - Provides connectivity between elements in a structural model
- **Default net type is a *wire***
 - E.g., wire noti0, noti1;
 - Any signal not in the input/output list or net declaration is assumed to be a wire
- **Other net types, used less frequently**
 - tri, triand, trior, wand, wor, supply0, supply1, ...
 - Only wire and tri supported by Quartus II

Verilog Variables

- Variables store values during program execution, but may not have physical significance
 - Common types are `reg` and `integer`
 - Variables are only used in *procedural code*
 - Procedural code can only assign values to variables
 - Variables cannot be changed from outside procedural code or from outside a module
- A *reg* variable may be a single bit or vector of bits
- An *integer* variable is a 32-bit (or larger) vector of bits interpreted as an integer

Verilog Vectors

- **Grouping of 1-bit signals**
 - `reg [7:0] byte1, byte2, byte3;`
 - `reg [1:16] Zbus;`
 - `wire [0:3] asel;`
- **Bit selection**
 - `byte1[5:2]` or `Zbus[3:7]`
- **Concatenation**
 - `{byte1,byte2}`
- **Bitwise Boolean operators**
 - `byte1 & byte2`
 - `Zbus | byte3` (pad on left with 0's)
- **Literals**
 - `7'b0011011`
 - `8'hA7`
- **Vectors are treated as unsigned integers**
 - Right-most bit is least significant
 - Independent of ascending or descending indexing

Arithmetic and Shift operators

- **Arithmetic**

- + Addition
 - Subtraction
 - * Multiplication
 - / Division
 - % Modulus

Beware!

**These can be expensive,
slow, or not synthesizable!**

- **Shift**

- << Shift left
 - >> Shift right

Conditionals

- **Logical Operators**

&& logical AND

|| OR

! logical NOT

== logical equality

!= logical inequality

> greater than

>= greater than or equal

< less than

<= less than or equal

- **Use these operators *only* in *conditional expressions* – *not* for Boolean operations**


Verilog programming styles

- **Structural**
 - Define explicit components and the connections between them
 - Textual equivalent of drawing a schematic
- **Dataflow**
 - Describe circuit in terms of *flow* of data and *operations* on that data
 - Uses *continuous-assignment* statements
- **Behavioral**
 - Write an algorithm that describes the circuit's output
 - May not be synthesizable or may lead to a very large circuit
 - Always useful for simulation

Structural Style

```
module V2to4dec( i0,i1,en,y0,y1,y2,y3 );  
  input i0,i1,en;  
  output y0,y1,y2,y3;  
  wire noti0,noti1;  
  
  not U1(noti0,i0);  
  not U2(noti1,i1);  
  and U3(y0,noti0,noti1,en);  
  and U4(y1,  i0,noti1,en);  
  and U5(y2,noti0,  i1,en);  
  and U6(y3,  i0,  i1,en);  
endmodule
```

 Direct correspondence
between Verilog and schematic



Dataflow Style

```
module V2to4decdf( i0,i1,en,y0,y1,y2,y3 );  
  input i0,i1,en;  
  output y0,y1,y2,y3;
```

```
  assign y0 = en & ~i0 & ~i1;  
  assign y1 = en & i0 & ~i1;  
  assign y2 = en & ~i0 & i1;  
  assign y3 = en & i0 & i1;  
endmodule
```

Note the correspondence
between Verilog and
Boolean logic

A new value is assigned to
the left hand side whenever
any value on the right hand
side changes

en	i0	i1	y3	y2	Y1	y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Behavioral Style

```
module V2to4decb( i0,i1,en,y0,y1,y2,y3 );
```

```
  input i0,i1,en;
```

```
  output y0,y1,y2,y3;
```

```
  reg y0,y1,y2,y3;
```

```
  always @ (en or i0 or i1)
```

```
  begin
```

```
    y0 = en & ~i0 & ~i1;
```

```
    y1 = en & i0 & ~i1;
```

```
    y2 = en & ~i0 & i1;
```

```
    y3 = en & i0 & i1;
```

```
  end
```

```
endmodule
```

- **Procedural code**
 - **But still very much in dataflow style**
- **Always block is key element of behavioral design**
- **Begin-end block groups sequences of procedural statements**
- **Note change of output to be reg variable – not a wire!**

Always Blocks

- Always blocks start execution whenever the value of one of the signals in the *sensitivity list* changes
 - Continues executing until there are no more changes in sensitivity list
- Always blocks execute *concurrently* with other always blocks, instances, and continuous assignments
 - Allows mixing of structural, dataflow and behavioral styles
- Procedural statements within an always block execute sequentially

Procedural Statements


- Procedural statements act a lot like regular programming language statements
 - Blocking assignment
 - *variable name = expression ;*
 - Nonblocking assignment
 - *variable name <= expression ;*
 - Begin-end blocks
 - *begin procedural-statement ... procedural-statement end*
 - If
 - *if (condition) procedural-statement else procedural-statement*
 - Case
 - *case (sel-expr) choice : procedural-statement ... endcase*
 - While
 - *while (logical-expression) procedural-statement*
 - Repeat
 - *Repeat (integer-expression) procedural-statement*

74x138 Decoder

```
module Vr74x138(G1, G2A_L, G2B_L, A, Y_L);  
    input G1, G2A_L, G2B_L;  
    input [2:0] A;  
    output [0:7] Y_L;  
    reg G2A,G2B;  
    reg [0:7] Y_L, Y;
```


<always block>

```
endmodule
```

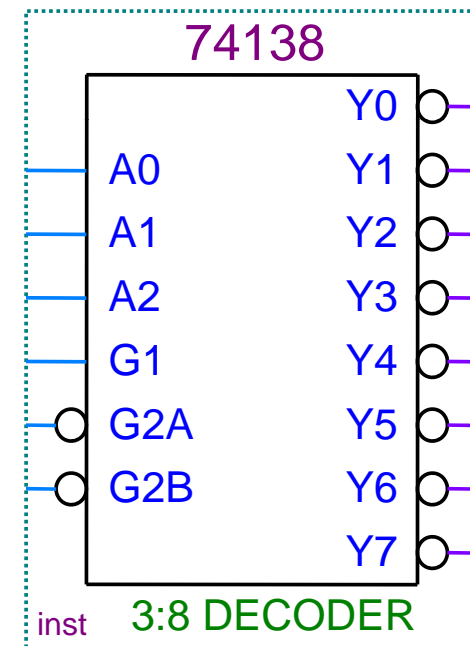

74x138 Decoder

```
always @ (G1 or G2A_L or G2B_L or A or Y) begin
    G2A = ~G2A_L; // convert inputs
    G2B = ~G2B_L;
    if ( G1 & G2A & G2B )
        case (A)
            0: Y = 8'b10000000;
            1: Y = 8'b01000000;
            2: Y = 8'b00100000;
            3: Y = 8'b00010000;
            4: Y = 8'b00001000;
            5: Y = 8'b00000100;
            6: Y = 8'b00000010;
            7: Y = 8'b00000001;
            default: Y = 8'b00000000;
        endcase
    else Y = 8'b00000000;
    Y_L = ~Y;      // convert outputs
end
```

 

Blocking vs Nonblocking

- **Blocking statement**

- E.g., $G2A = \sim G2A_L$;
- Assignment is *immediate*; i.e., following statements are blocked until after the assignment

- **Nonblocking statement**

- E.g., $A \leq B \ \& \ C$;
- Assignment is *delayed* until after execution of always block is completed

```
always  
begin  
  A = B;  
  B = A;  
end
```

$A = B, B = B$

```
always  
begin  
  A <= B;  
  B <= A;  
end
```

Swap A, B

Coding Rules*

- Always use **blocking** assignments in **always blocks** intended to create **combinational** logic
- Always use **nonblocking** assignments in **always blocks** intended to create **sequential** logic
- Do not **mix** blocking and nonblocking assignments in the same **always block**
- Do not make assignments to the same variable in two **different always blocks**

***Very strongly suggested recommendations**

Inferred Latches

- You should *always* assign a value to a variable on every path through an always block
- If you don't, then
 - the simulator infers that you don't want the value of the variable to change,
 - and “infers a latch” to store the value of the variable for the next execution of the block
- **Avoiding inferred latches**
 - Always assign *default* values to *all* variables at the start of the always block
 - Multiple assignments to the same variable in an always block is allowed (*last* assignment used)

Sensitivity Lists

- It's easy to leave a net or variable out of the always block sensitivity list
- Simulator will simulate statements *as given*
 - Behavior become partially *sequential*, not purely *combinational*
- Synthesizer ignores the error
 - Synthesizes the intended combinational circuit
- You could end up with *different* results from the simulator and the synthesizer!
 - Verilog-2001 allows: always @ *

74x148 Priority Encoder

```
module Vr74x148(EI_L, I_L, A_L, EO_L, GS_L);
```

```
  input EI_L;
```

```
  input [7:0] I_L;
```

```
  output [2:0] A_L;
```

```
  output EO_L, GS_L;
```

```
  reg [7:0] I;
```

```
  reg [2:0] A,A_L;
```

```
  reg EI, EO_L, EO, GS_L, GS;
```

```
  integer j;
```

```
  always @ (EI_L or EI or I_L or I or A or EO or GS) begin
```

```
    EI = ~EI_L; I = ~I_L;
```

```
    // convert inputs
```

```
    EO_L = ~EO; GS_L = ~GS; A_L = ~A; // convert outputs
```

```
    EO = 1; GS = 0; A = 0;
```

```
    // default output values
```

```
  begin
```

```
    if (EI==0) EO = 0;
```

```
    else for (j=0; j<=7; j=j+1)
```

```
      if (I[j]==1)
```


```
        begin GS = 1; EO = 0; A = j; end
```

```
    end
```

```
  end
```

```
endmodule
```

Inputs										Outputs				
EI_L	I0_L	I1_L	I2_L	I3_L	I4_L	I5_L	I6_L	I7_L		A2_L	A1_L	A0_L	GS_L	EO_L
1	x	x	x	x	x	x	x	x		1	1	1	1	1
0	x	x	x	x	x	x	x	0		0	0	0	0	1
0	x	x	x	x	x	x	0	1		0	0	1	0	1
0	x	x	x	x	x	0	1	1		0	1	0	0	1
0	x	x	x	x	0	1	1	1		0	1	1	0	1
0	x	x	x	0	1	1	1	1		1	0	0	0	1
0	x	x	0	1	1	1	1	1		1	0	1	0	1
0	x	0	1	1	1	1	1	1		1	1	0	0	1
0	0	1	1	1	1	1	1	1		1	1	1	0	1
0	1	1	1	1	1	1	1	1		1	1	1	1	0

 

Seven Segment Decoder

- Converts 4-bit input to HEX character

```
module seven_seg(B,Y);  
    input [3:0] B;  
    output [0:6] Y;  
    reg [0:6] Y;
```

```
    ...  
endmodule
```

- Hex digits 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F
- Bits of Y are drivers for segments a,b,c,d,e,f,g
- Segments are driven with a logic LOW

Seven Segment Display Architecture

Behavioral architecture

- Encodings of all 16
HEX digits

```
always @ (B)
```

```
case (B)
```

```
4'b0000 : Y = 7'b0000001;
```

```
4'b0001 : Y = 7'b1001111;
```

```
4'b0010 : Y = 7'b0010010;
```

```
4'b0011 : Y = 7'b0000110;
```

```
4'b0100 : Y = 7'b1001100;
```

```
4'b0101 : Y = 7'b0100100;
```

```
4'b0110 : Y = 7'b0100000;
```

```
4'b0111 : Y = 7'b0001111;
```

```
4'b1000 : Y = 7'b0000000;
```

```
4'b1001 : Y = 7'b0001100;
```

```
4'b1010 : Y = 7'b0001000;
```

```
4'b1011 : Y = 7'b1100000;
```

```
4'b1100 : Y = 7'b0110001;
```

```
4'b1101 : Y = 7'b1000010;
```

```
4'b1110 : Y = 7'b0110000;
```

```
4'b1111 : Y = 7'b0111000;
```

```
default : Y = 7'b1111111;
```

```
endcase
```


Before Next Class

- Read sections 8.1, 8.4-8.5

Next time

Registers

Counters

Shift Registers